

Square Root Operation.

Fixed Point Square Root Operation

Henry Córdoba Marin

Escuela de Ingeniería Eléctrica y Electrónica
Universidad del Valle

Square Root Operation.

Abstract

Square root operation is considered a difficult operation to implement in hardware, will present a FPGA implementation of a 32 bit fixed-point square root based on the non-restoring algorithm square root.

The Non-Restoring Algorithm

This algorithm uses the two's complement representation for the square root result, at each iteration the algorithm can generate an exact result value even in the last bit. there is not need to do the complex calculation as other methods. The exact remainder can be obtained immediately (with a little correction if it is negative). Assume that the radicand is an 32-bit unsigned number (denoted by $D[31..0]$).

The square root is denoted by $Q[15..0]$. R is the remainder ($R = D - (Q^2)$) which will be denoted by $R[16..0]$

Square Root Operation.


Hardware Design

The circuit was designed to use two shift registers (one is a shift 1-bit left, the other is shift 2-bit left), one normal register, and an adder. D is the radicand, Q is the solution and R is the remainder.

The size of each register (D, Q and R) and ALU can be determined by the size of radicand register. If the radicand contains X bits, Q will be $X/2$, while ALU and R would be $(X/2)+2$ bits, and the iteration total number is $(x/2)+1$ cycles. In each cycle D will be shifted left 2 bits and Q will be shifted left 1 bit. The start up value of register Q and R is "0" and should be clear once the radicand is loaded into register D.

Square Root Operation.

Datapath

 

Algorithm

D be 32-bit unsigned integer
Q be 16-bit unsigned interger (Result)
R be 17-bit integer ($R = D - Q^2$)

Algorithm

$Q=0; R=0;$

for $i=15$ to 0 do

if ($R \geq 0$)

$R = (R \ll 2) \text{ or } (D \gg (i+i) \& 3);$

$R = R - ((Q \ll 2) \text{ or } 1);$

Else

$R = (R \ll 2) \text{ or } (D \gg (i+i) \& 3);$

$R = R - ((Q \ll 2) \text{ or } 3);$

End if

if ($R \geq 0$)

$Q = (Q \ll 1) \text{ or } 1;$


Else

$Q = (Q \ll 1) \text{ or } 0;$

End if

Square Root Operation.

Really Datapath

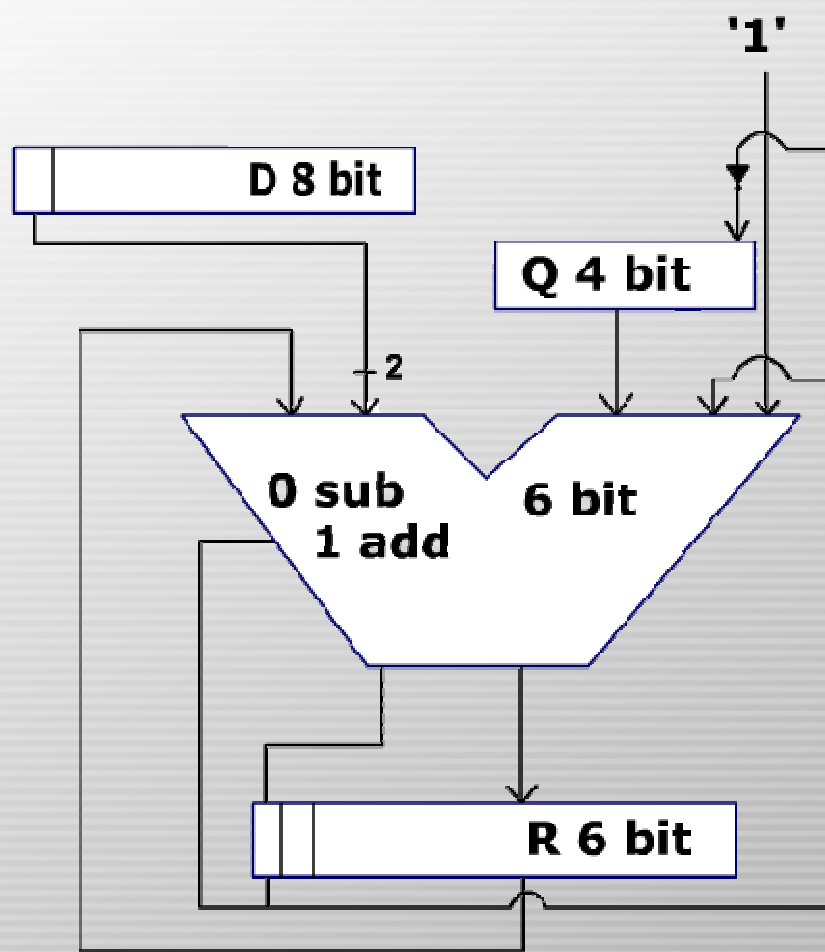

Algorithm Rewrite

D be 8-bit unsigned integer
Q be 4-bit unsigned integer (Result)
R be 5-bit integer ($R = D - Q^2$)

Algorithm

$Q=0; R=0;$

for $i=3$ to 0 do

if ($i=3$)

$R = R \text{ or } (D \& 192);$

else

$R = (R \ll 2) \text{ or } ((D \ll 2) \& 192);$

if ($R \geq 0$)

$R = R - ((Q \ll 2) \text{ or } 1); Q = (Q \ll 1)$

$Q = Q \text{ or } 1;$

Else


$R = R - ((Q \ll 2) \text{ or } 3); Q = (Q \ll 1)$

$Q = Q \text{ or } 0;$

End if


Square Root Operation.

ASM

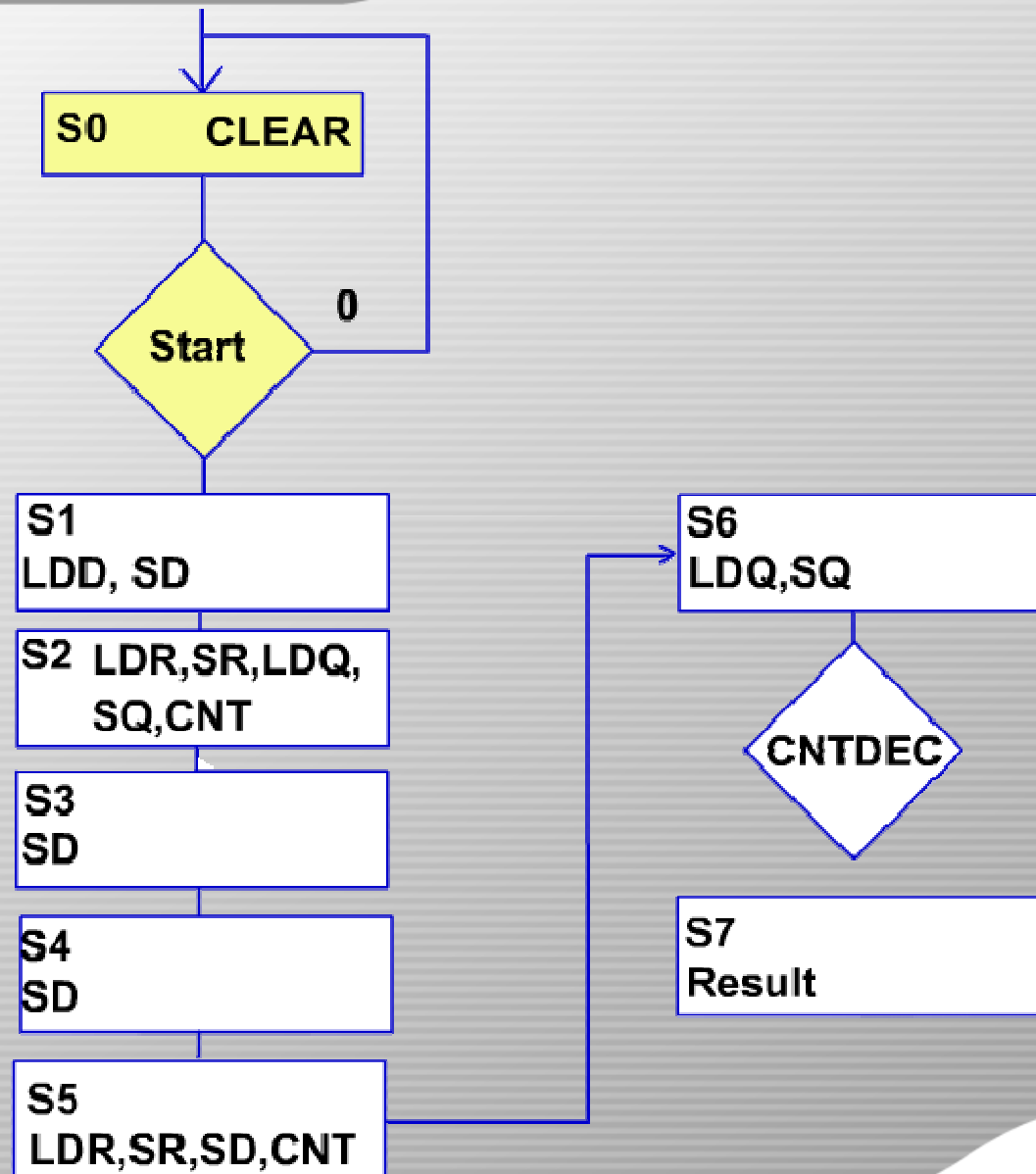


Square Root Operation.

ASM

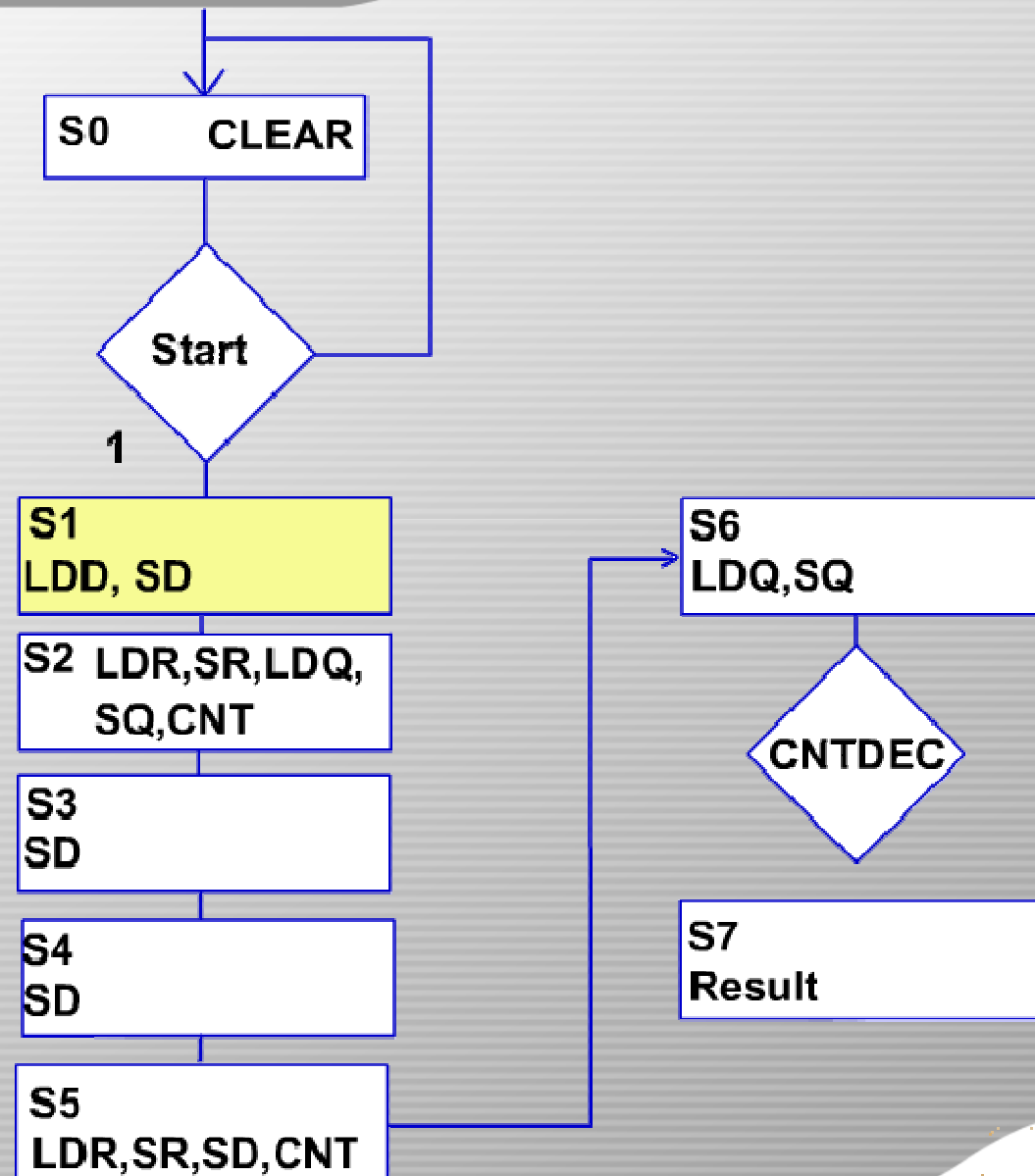


Square Root Operation.

ASM

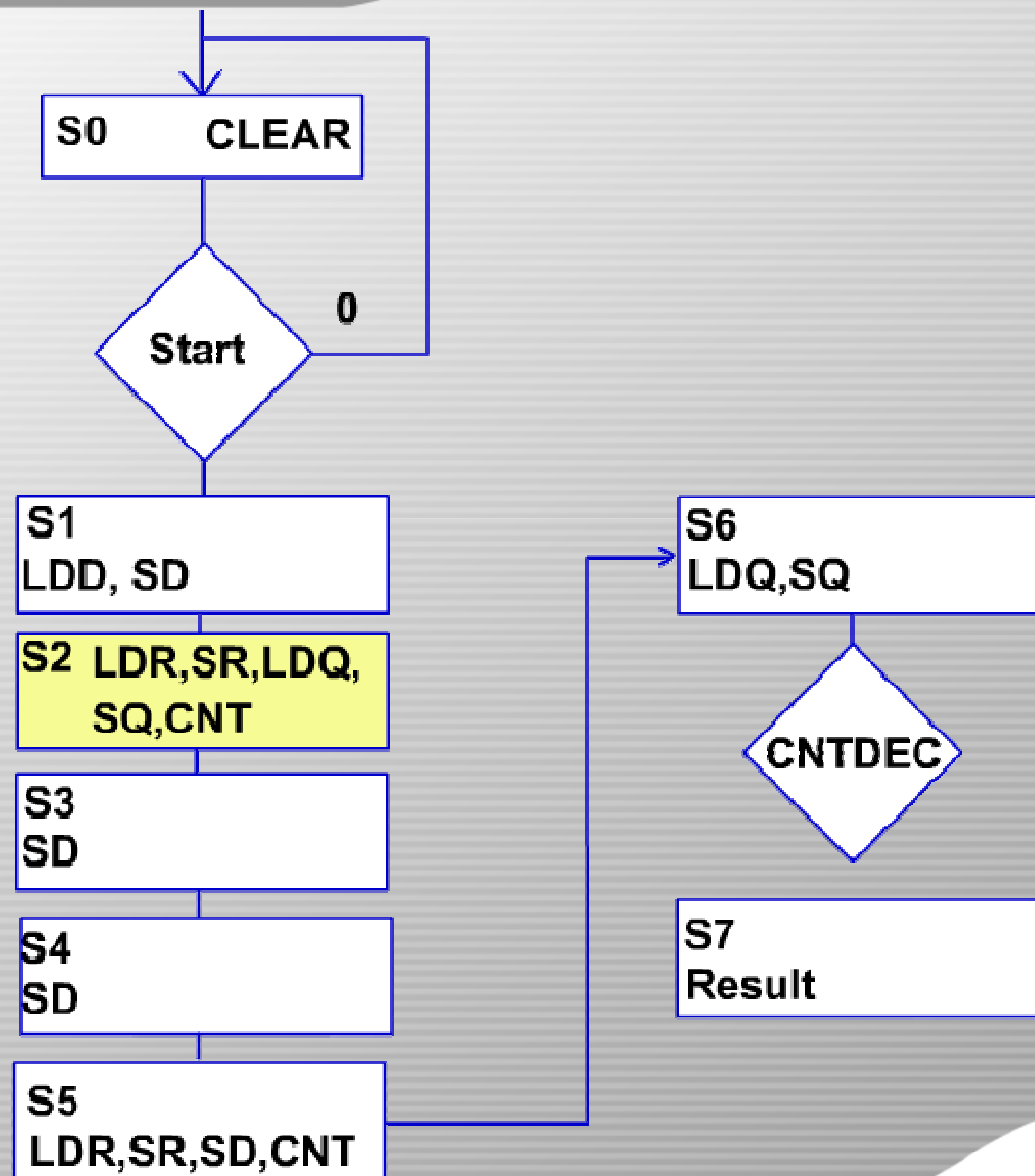


Square Root Operation.

ASM

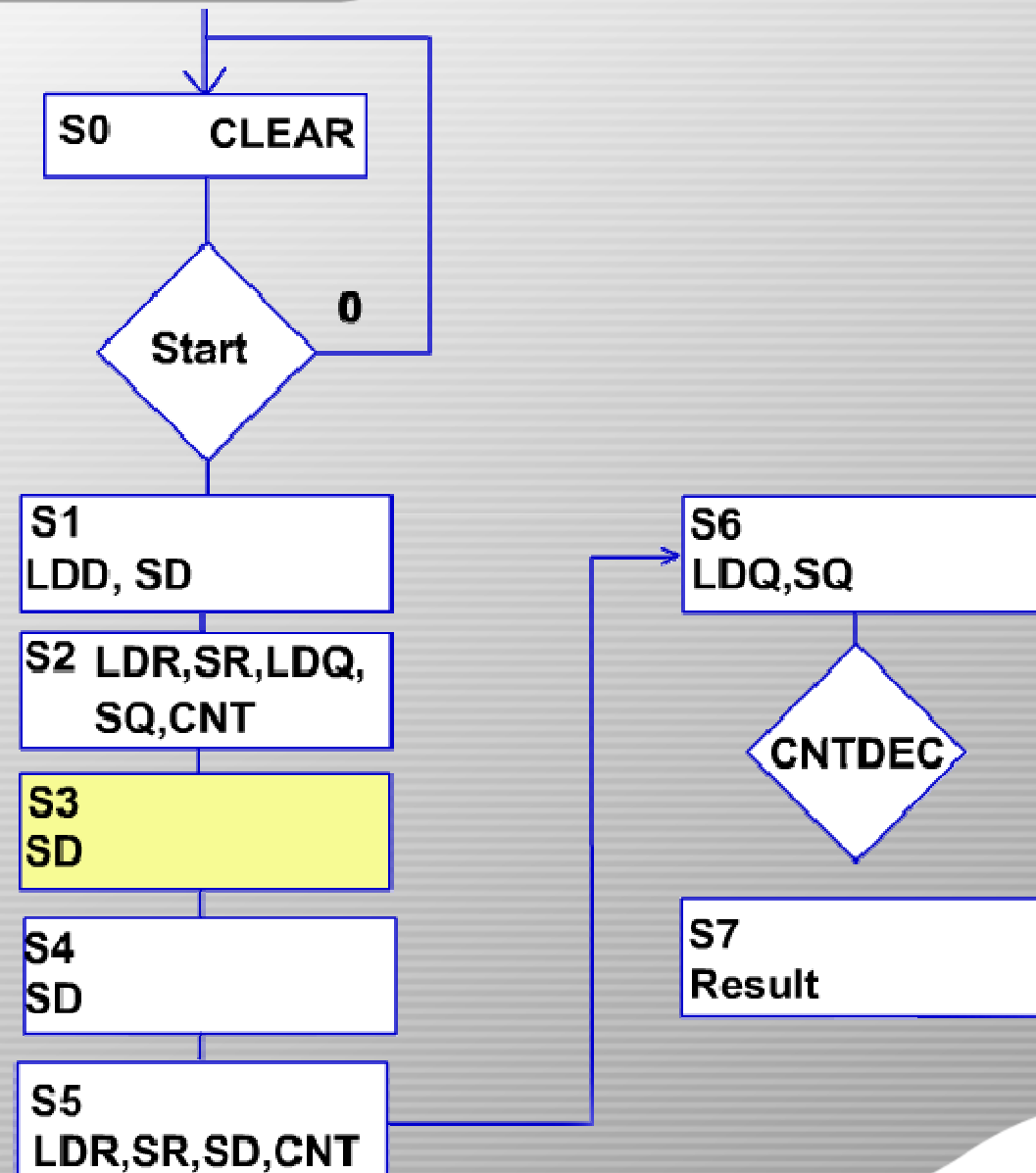


Square Root Operation.

ASM

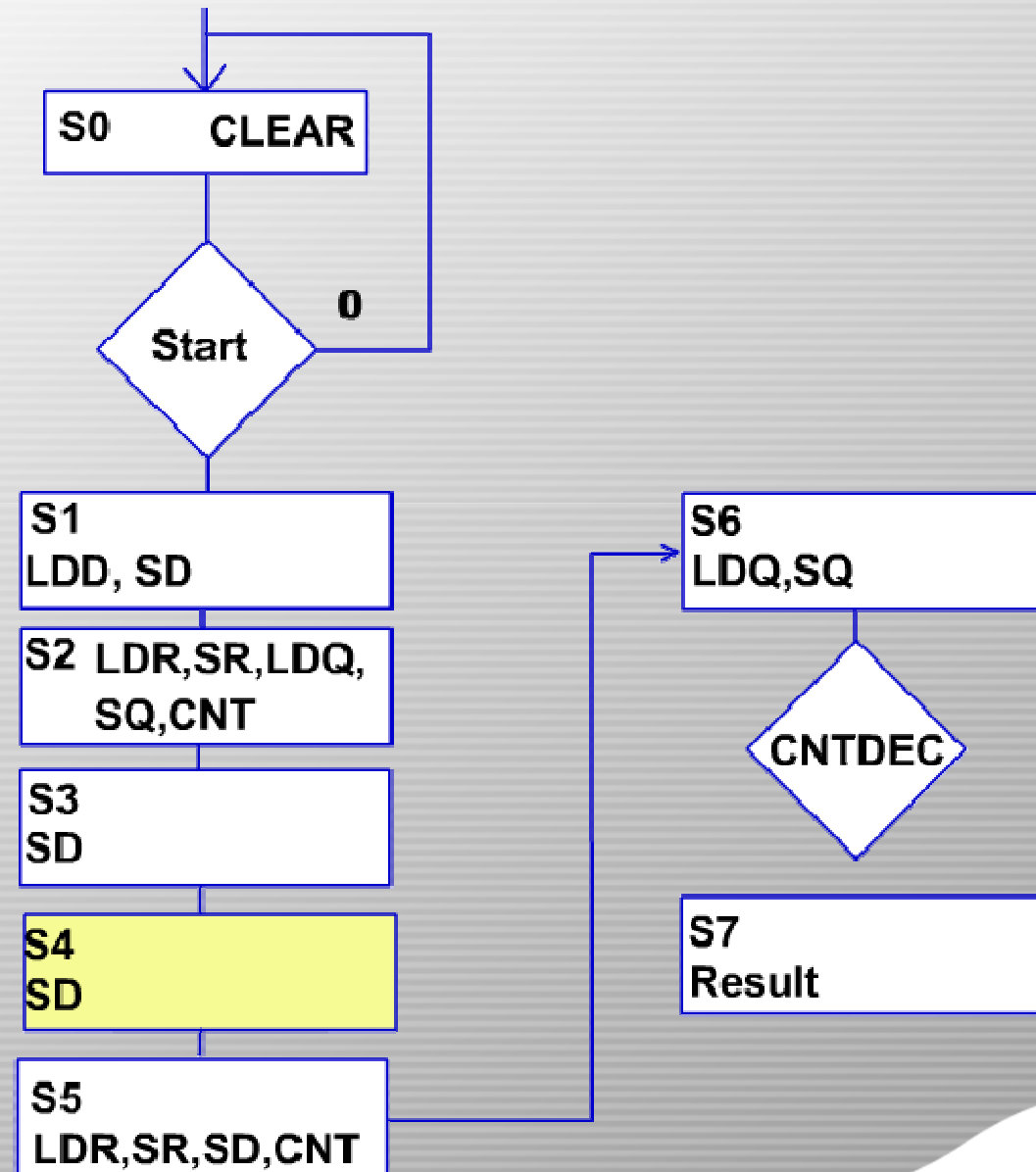


Square Root Operation.

ASM

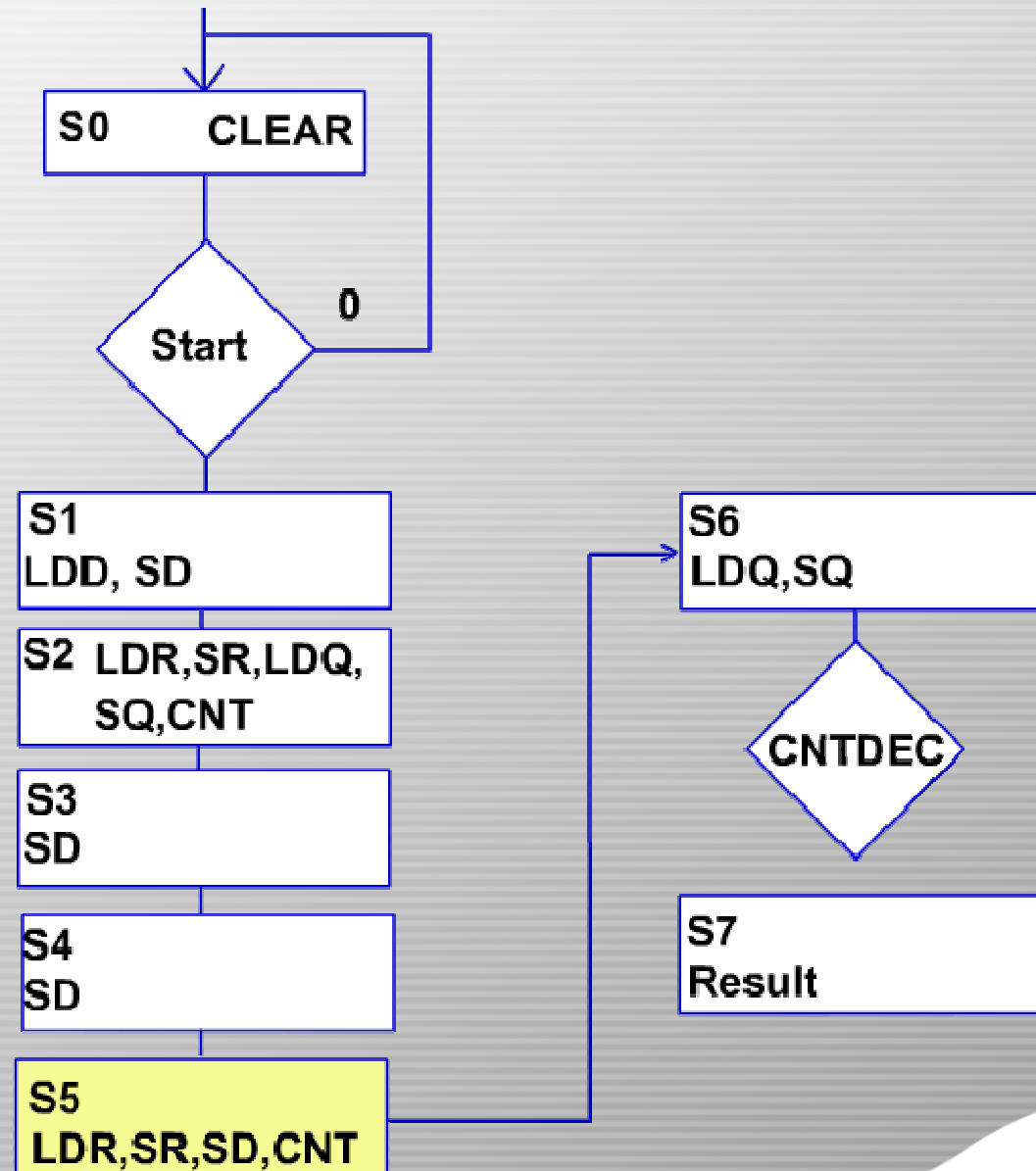


Square Root Operation.

ASM

 


Square Root Operation.

ASM

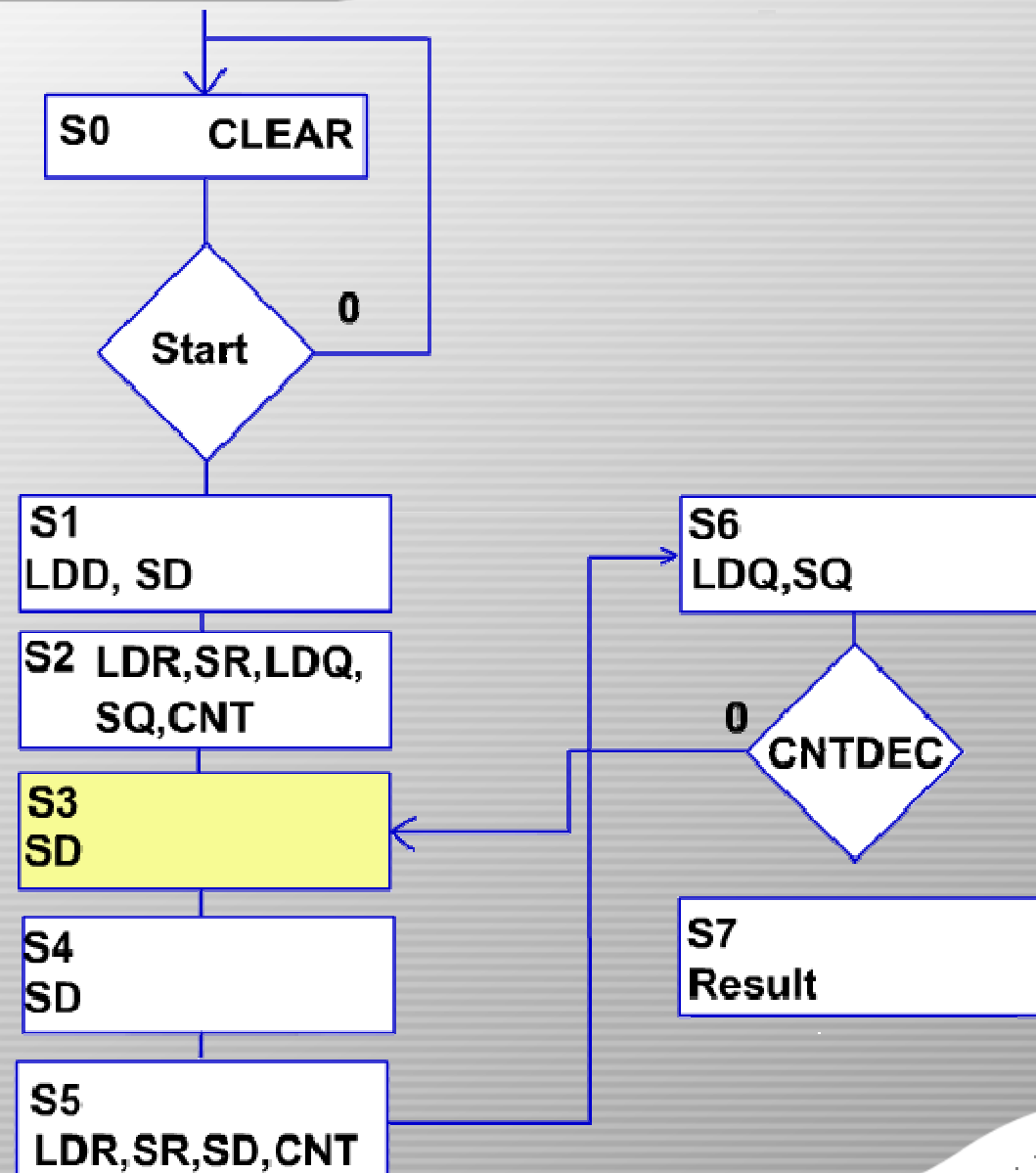


Square Root Operation.

ASM

 


Square Root Operation.

ASM

 


Square Root Operation.

ASM

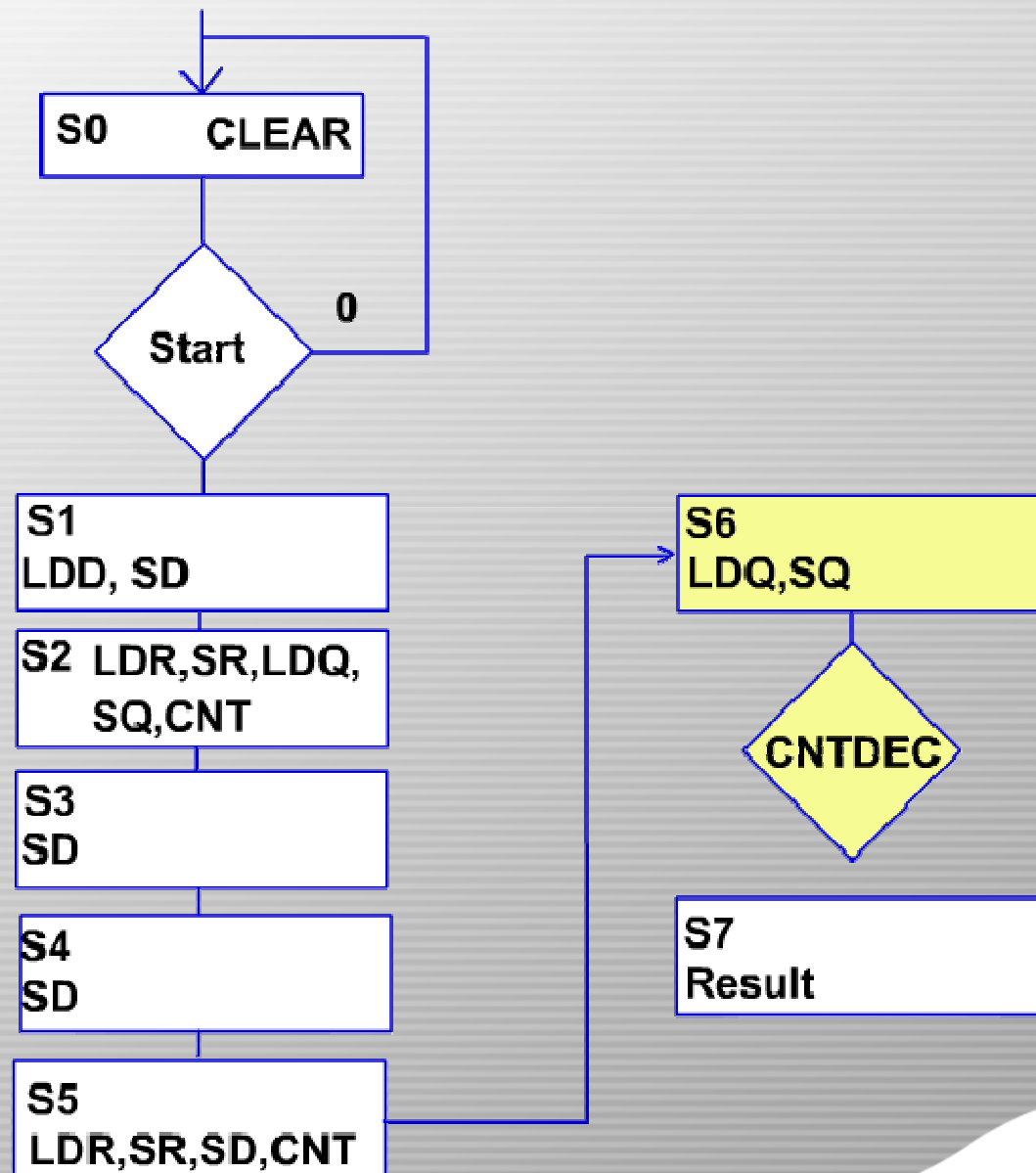

Square Root Operation.


ASM

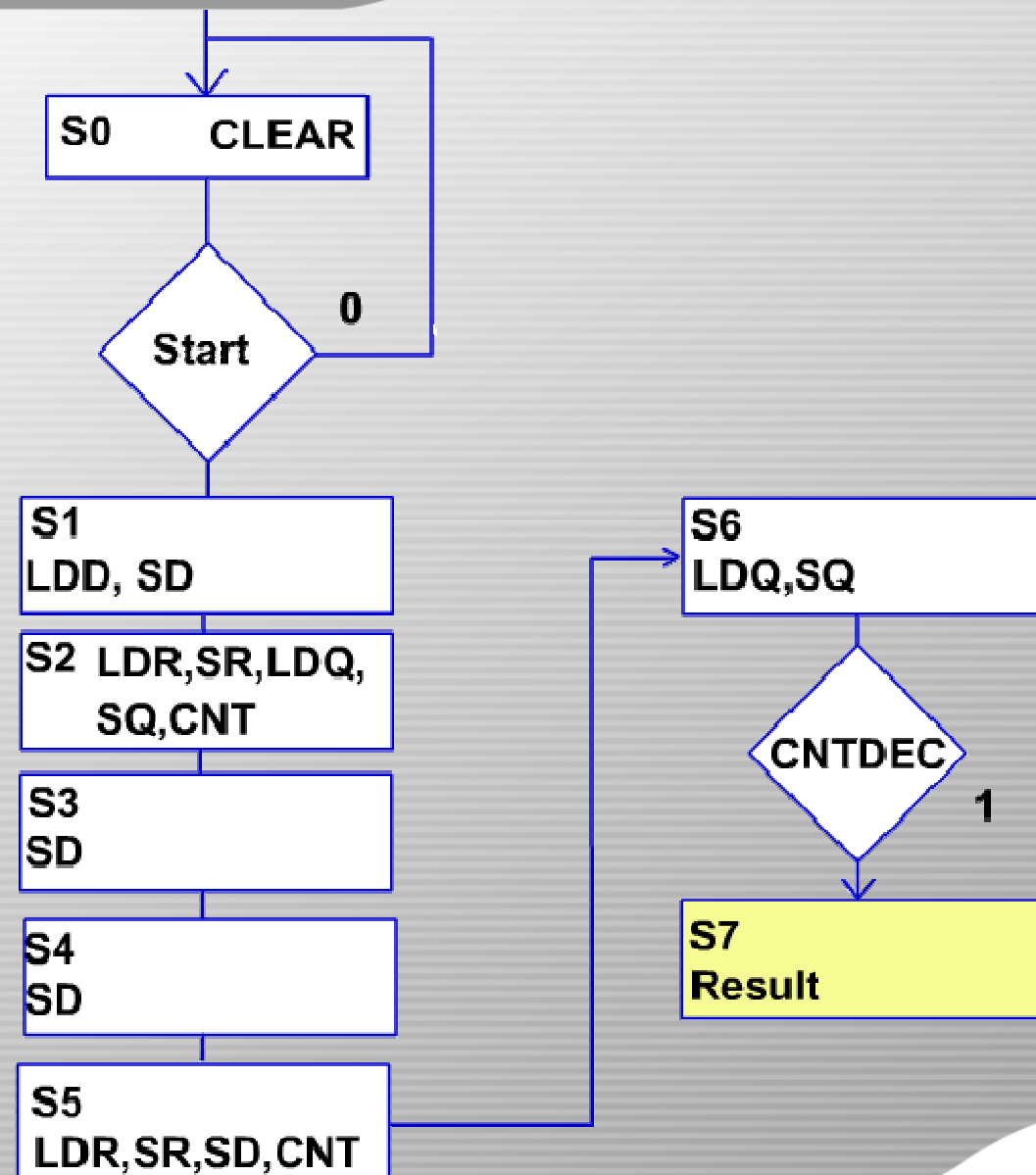

Square Root Operation.

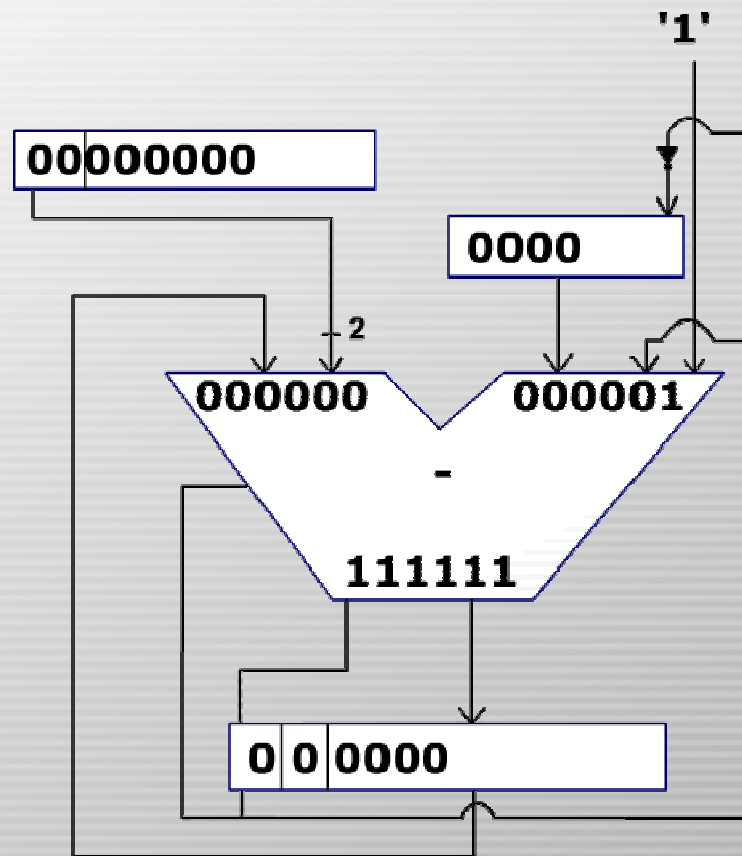Example

The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).




Start set R=000000 and Q=0000

Square Root Operation.

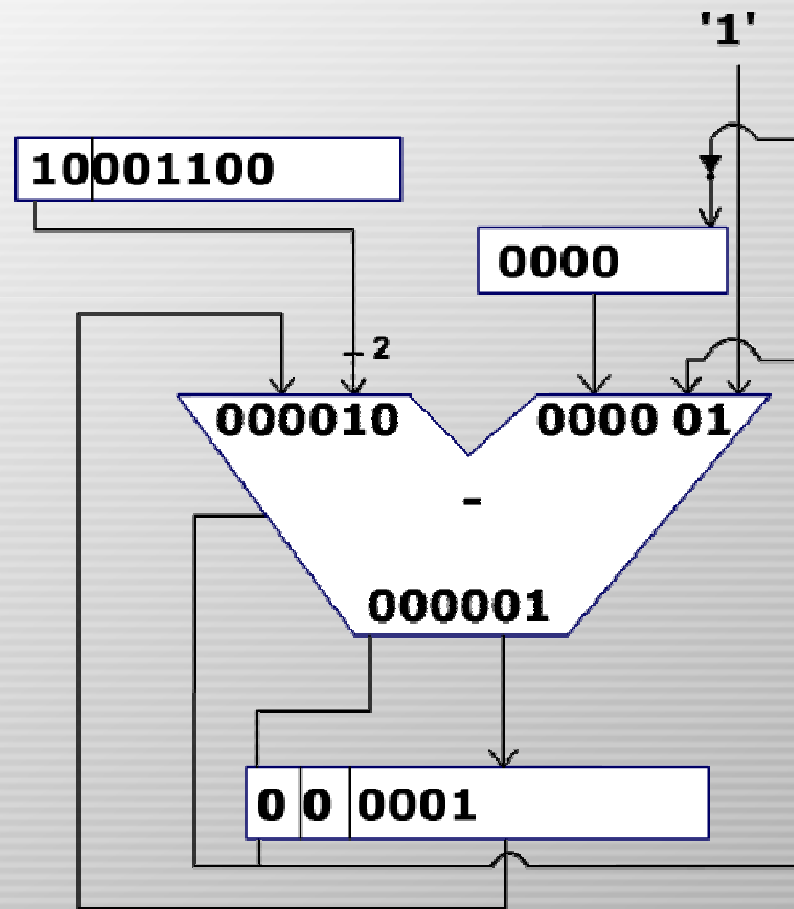Example

The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).




$D = 10001100$
 $R = R \text{ or } (D \ \& \ 192)$
 $R = R - (Q \text{ or } 1)$

Square Root Operation.

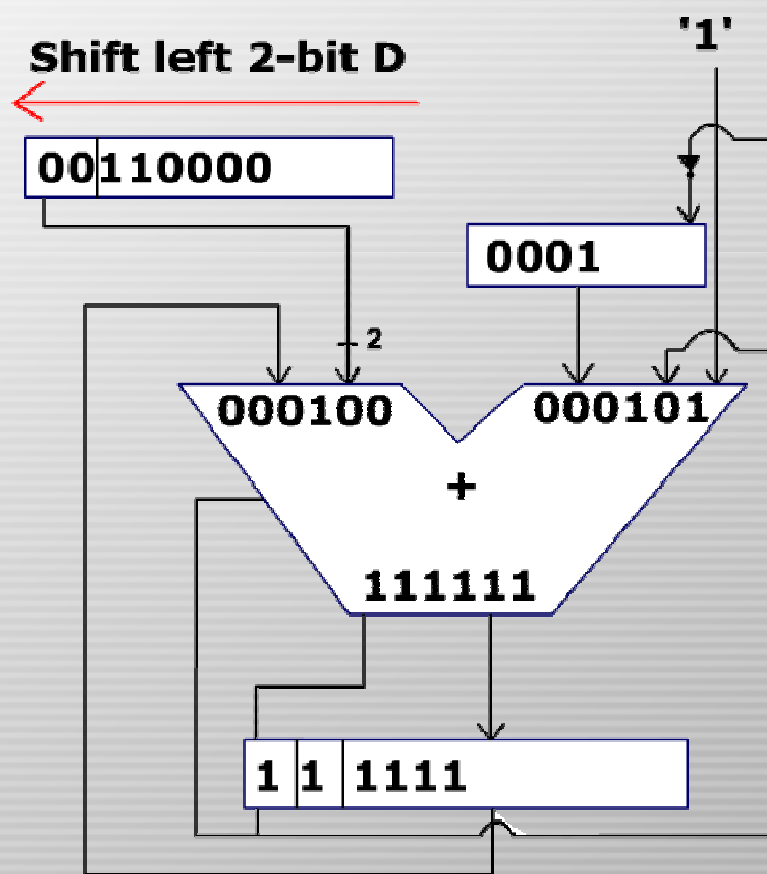Example

The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



$$Q = (Q \text{ or } 1)$$


$$R = (R \ll 2) \text{ or } ((D \ll 2) \& 192)$$

$$R = R - (Q \text{ or } 1)$$

Square Root Operation.

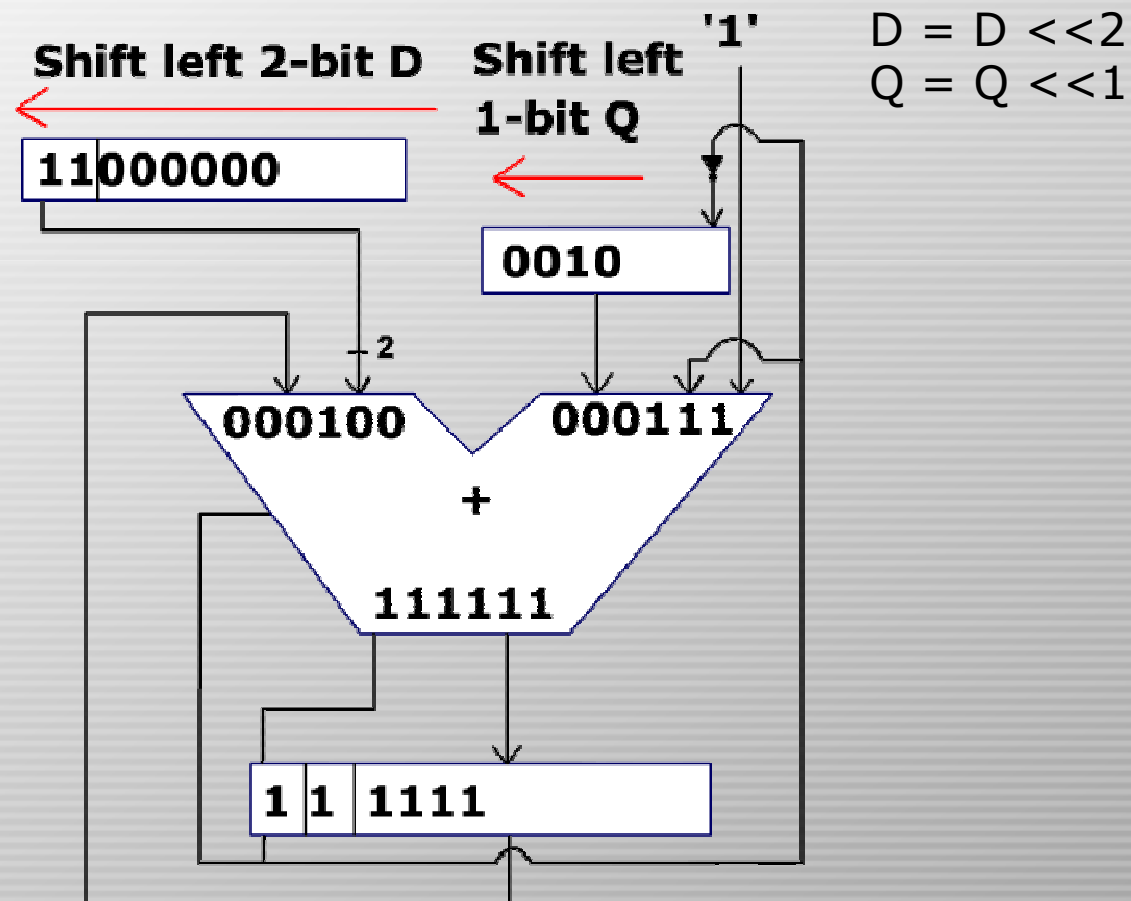Example


The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



Square Root Operation.

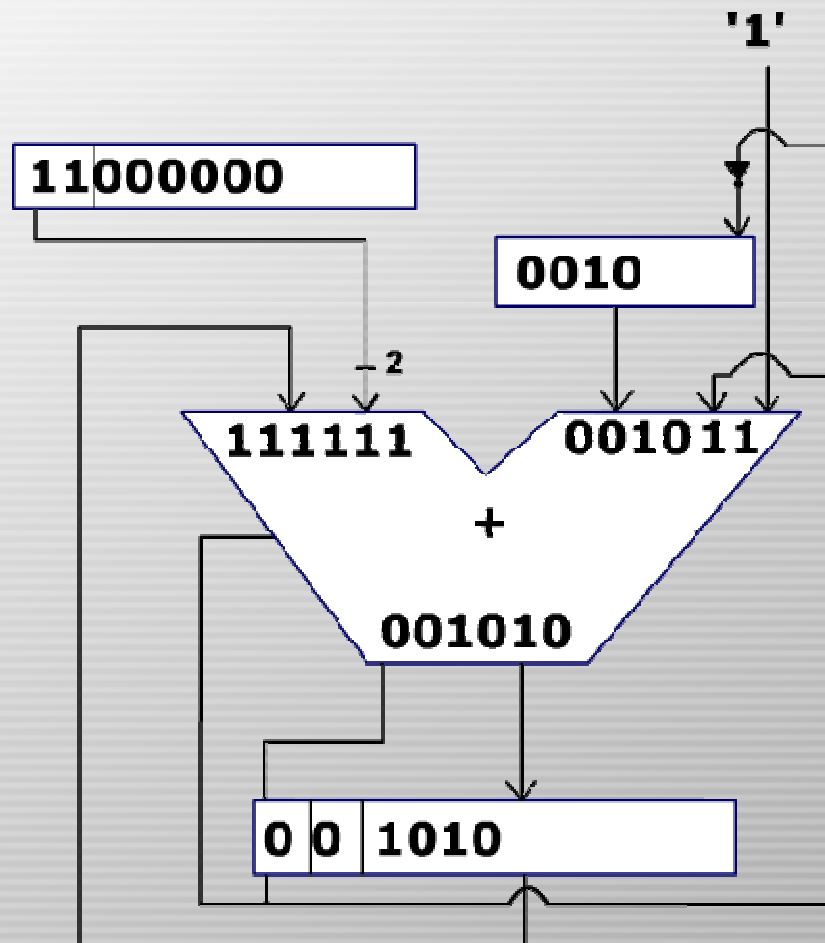Example

The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



$Q = Q \text{ or } 0$


$R = (R \ll 2) \text{ or } ((D \ll 2) \& 192)$

$R = R + (Q \text{ or } 3)$

Square Root Operation.

 Example


The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



Square Root Operation.

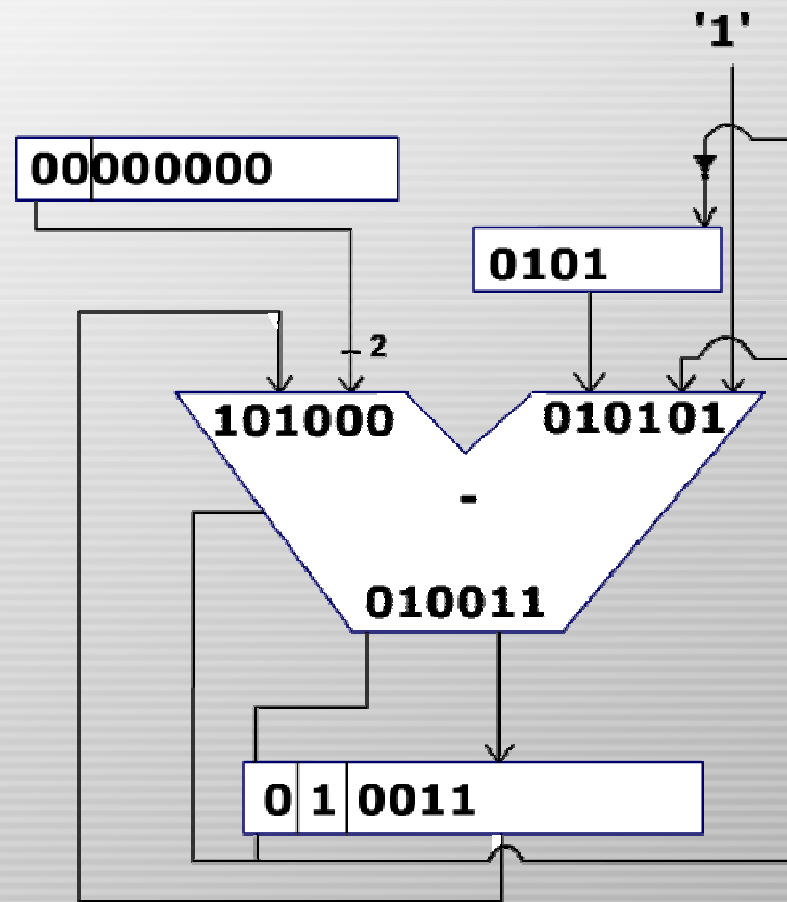Example

The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



$Q = Q \text{ or } 1$


$R = (R \ll 2) \text{ or } ((D \ll 2) \& 192)$

$R = R - (Q \text{ or } 1)$

Square Root Operation.

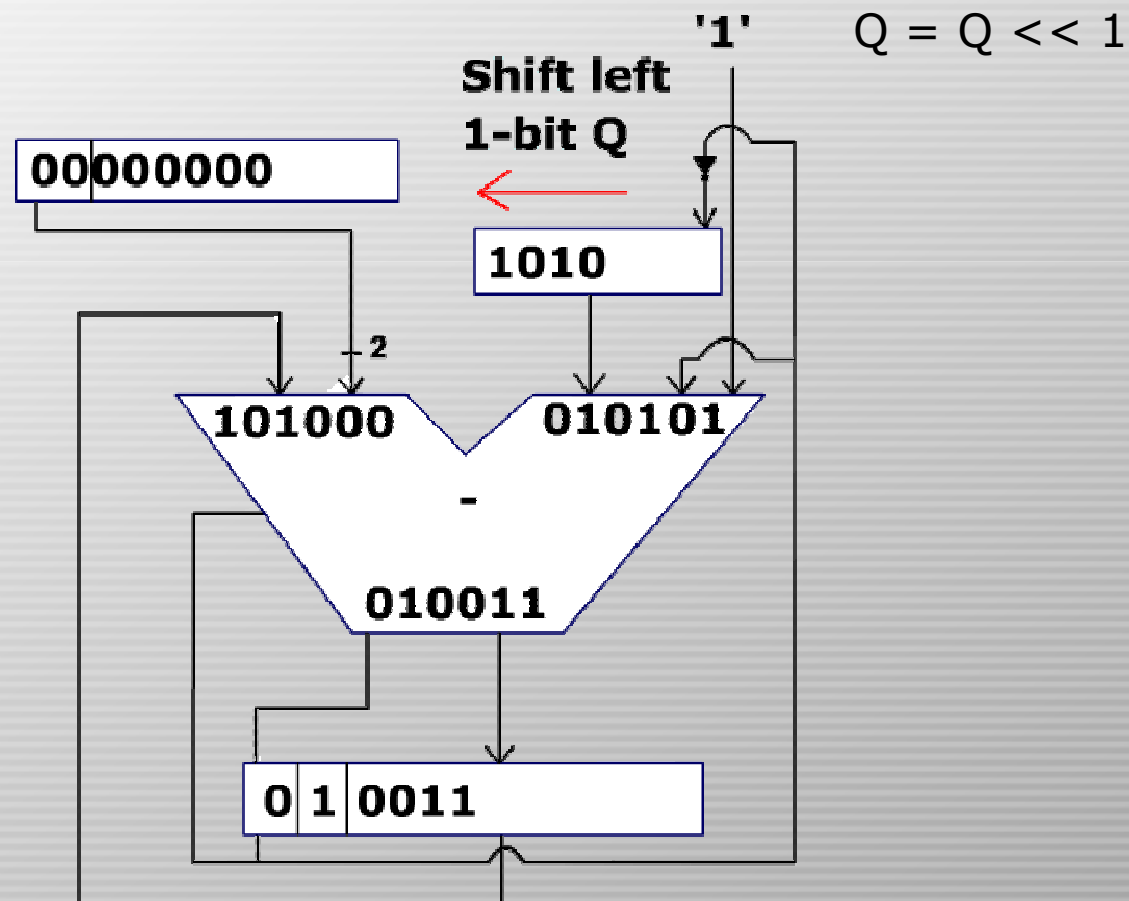Example


The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



Square Root Operation.

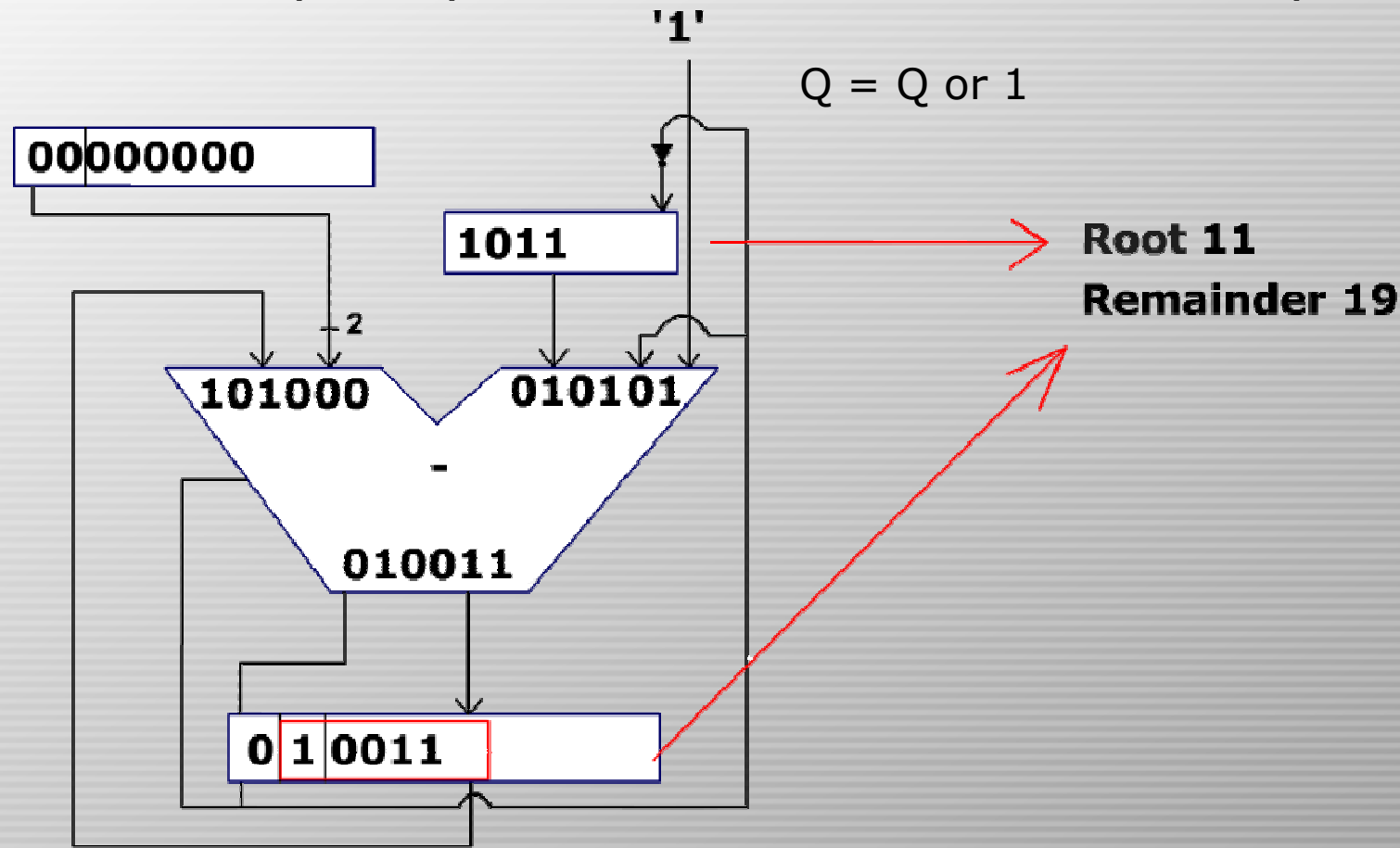Example

The Radincand is a number of 8 bits 140 (10001100₂), the solution Q should be 11 (1011₂), and the remainder R should be 19 (10011₂).



Square Root Operation.

The Circuit

Using MAX-PLUS design tools , the circuit was test.
To this circuit was used the follow devices:

74198 8-bit Shift Register

74194 4-bit Shift Register


6-bit Register maked with megafunction

Add-Sub maked with megafunction

4-bit Counter down maked with megafunction

Fsm maked in AHDL

Some gates.

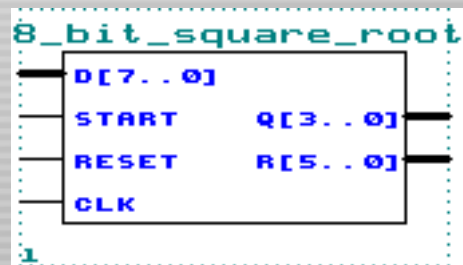

Square Root Operation.

The FSM

```
SUBDESIGN fsm
```

```
(
```

```
  clk, reset  : INPUT;
```

```
  start, cnt  : INPUT;
```

```
  LDD, SD, LDR, SR, LDQ, SQ, CLEAR, CNTD : OUTPUT
```

```
)
```

```
VARIABLE
```

```
  ss: MACHINE OF BITS (LDD, SD, LDR, SR, LDQ, SQ, CLEAR, CNTD)
```

```
  WITH STATES (
```

```
    s0 = B"00000000",
```

```
    s1 = B"11000010",
```

```
    s2 = B"00111111",
```

```
    s3 = B"01000010",
```

```
    s4 = B"01000010",
```

```
    s5 = B"00110111",
```

```
    s6 = B"00001110",
```

```
    s7 = B"00000010");
```

Square Root Operation.

The FSM

BEGIN

ss.clk = clk;

ss.reset = reset;

TABLE

ss, start, cnt => ss;

s0, 0, x => s0;

s0, 1, x => s1;

s1, x, x => s2;

s2, x, x => s3;

s3, x, x => s4;

s4, x, x => s5;

s5, x, x => s6;

s6, x, 0 => s3;

s6, x, 1 => s7;

s7, 0, 1 => s7;


s7, 1, 1 => s0;

END TABLE;

END;


Square Root Operation.

Example 81

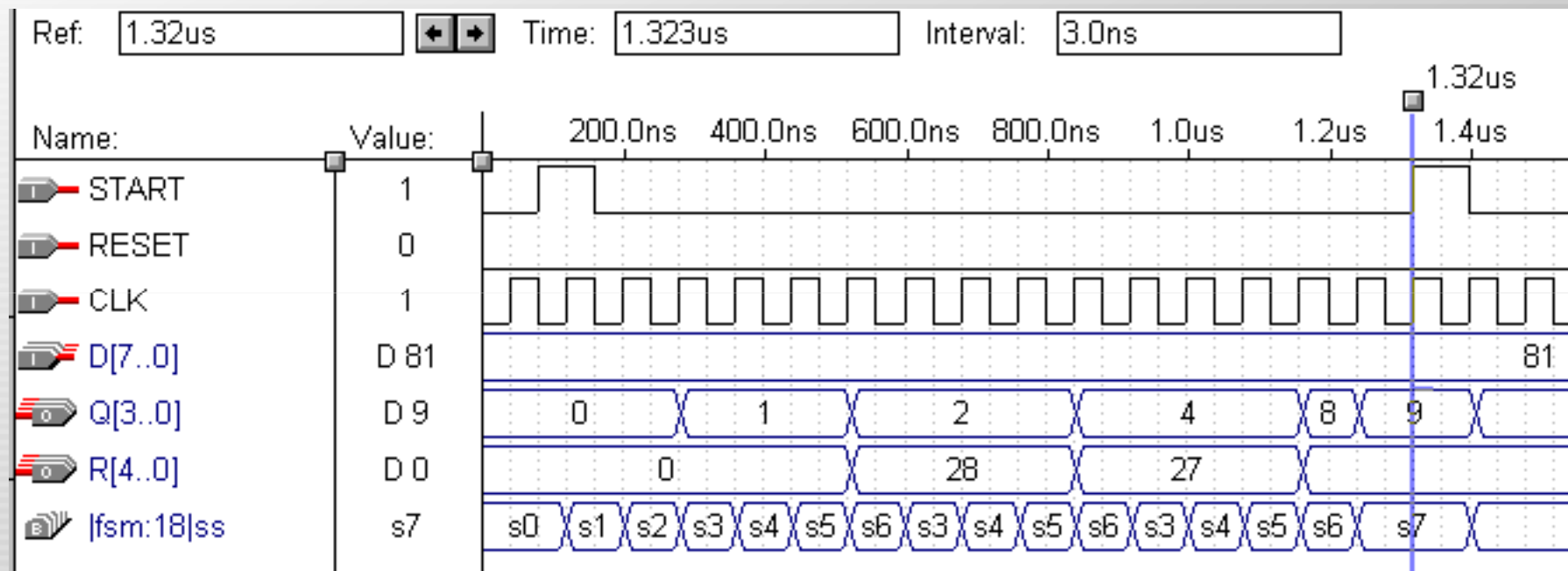


Square Root Operation.

Example 140

 


Square Root Operation.

Example 169

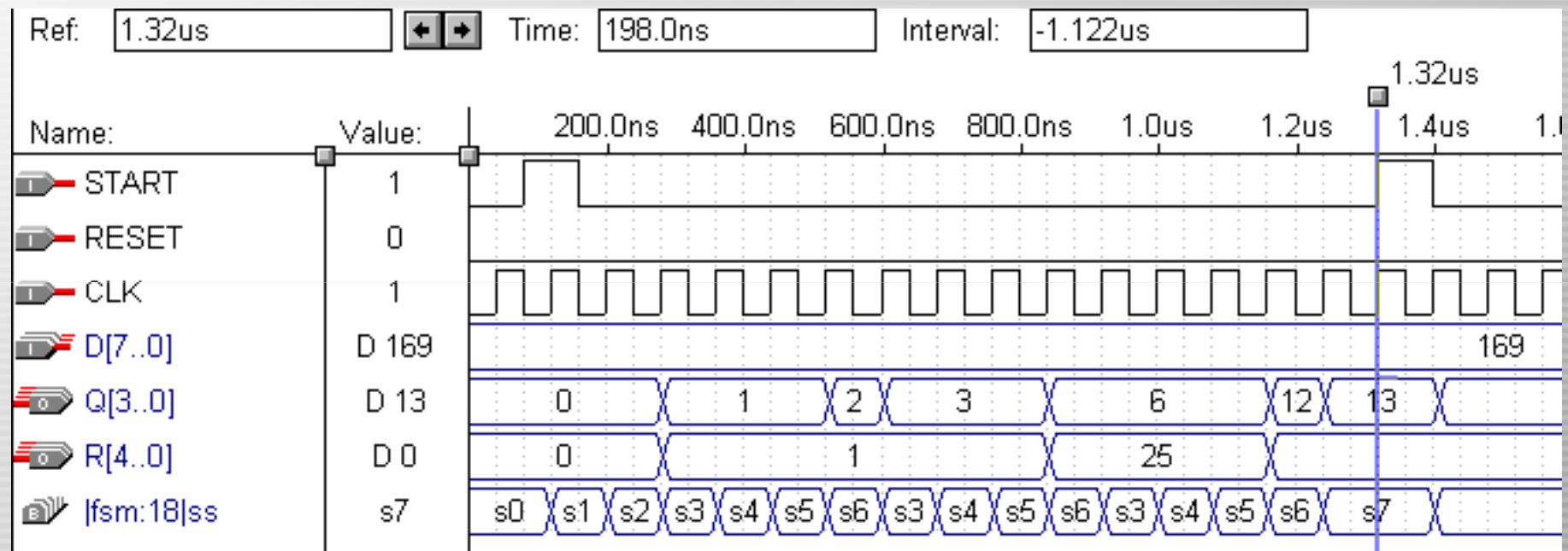

Square Root Operation.

Example 255

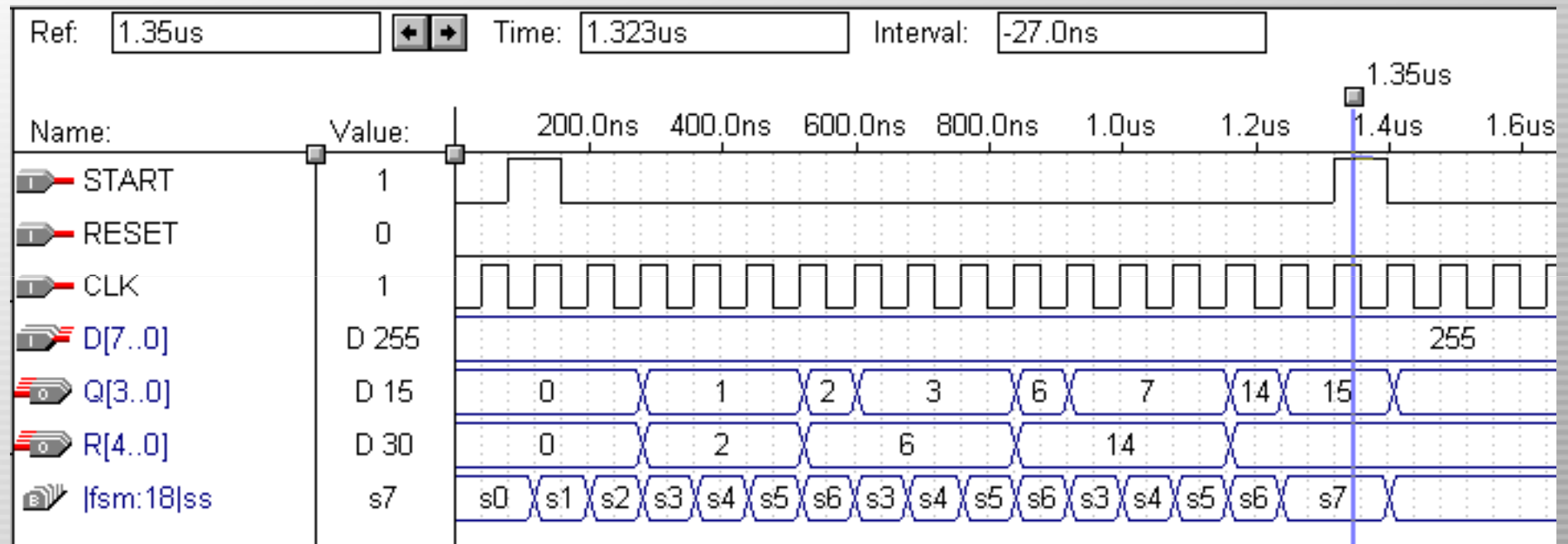

Square Root Operation.

References

An FPGA Implementation on a Fixed-Point Square Root Operation
K. Piromsopa, C. Apornthewan and P. Chongsatitvatana

hecomain@hotmail.com